

Cs223-03

Lab03

Osman Buğra Aydın

21704100

25 October 2020

B-) Behavioral SystemVerilog module for 2-to-4 decoder

```
`timescale 1ns / 1ps module BehavioralTwoToFourDecoder( input a0, a1, output b0, b1, b2, b3 ); assign b0 = a0 \& a1; assign b1 = a0 \& \sim a1; assign b2 = \sim a0 \& a1; assign b3 = \sim a0 \& \sim a1;
```

Testbench

endmodule

```
`timescale 1ns / 1ps
module BehavioralTwoToFourDecoder_tb;

reg a0, a1;
wire b0, b1, b2, b3;

BehavioralTwoToFourDecoder
uut( .a0(a0), .a1(a1), .b0(b0), .b1(b1), .b2(b2), .b3(b3) );

initial
begin
#300

#30; a0 = 0; a1 = 0;
#30; a0 = 1; a1 = 0;
#30; a0 = 0; a1 = 1;
#30; a0 = 1; a1 = 1;
end
```

C-) Behavioral SystemVerilog module for 4-to-1 multiplexer


```
`timescale 1ns / 1ps
module BehavioralFourToOneMux(input a0, a1, a2, a3, input s0, s1,
output y );
  assign y = a0 & (\sim s0 & \sim s1) | a1 & (s0 & \sim s1) | a2 & (\sim s0 & s1) | a3
& (s0 & s1);
endmodule
Testbench
`timescale 1ns / 1ps
module BehavioralFourToOneMux tb;
  reg a0, a1, a2, a3, s0, s1;
  wire y;
  BehavioralFourToOneMux uut
(.a0(a0), .a1(a1), .a2(a2), .a3(a3), .s0(s0), .s1(s1), .y(y));
  initial
     begin
       #300
       #30; a0=1; a1=0; a2=0; a3=0; s0=0; s1=0;
       #30; a0=0; a1=1; a2=0; a3=0; s0=1; s1=0;
       #30; a0=0; a1=0; a2=1; a3=0; s0=0; s1=1;
       #30; a0=0; a1=0; a2=0; a3=1; s0=1; s1=1;
```

endmodule

end

D-) Structural Module of 8-to-1 MUX

Schematic

 

SystemVerilog


```
`timescale 1ns / 1ps
module MuxEightToOne( input a0, a1, a2, a3, a4, a5, a6, a7, input s0, s1, s2, output y );
  wire w0, w1, w2, w3, w4;
  BehavioralFourToOneMux mux0( a0, a1, a2, a3, s0, s1, w0 );
  BehavioralFourToOneMux mux1( a4, a5, a6, a7, s0 ,s1, w1 );
  not not0( w2, s2);
  and and0( w3, w0, w2 );
  and and1( w4, w1, s2 );
  or or0( y, w3, w4 );
```

Testbench

```
`timescale 1ns / 1ps
module MuxEightToOne tb;
        reg a0, a1, a2, a3, a4, a5, a6, a7;
        reg s0, s1, s2;
        wire y;
        MuxEightToOne
uut(.a0(a0), .a1(a1), .a2(a2), .a3(a3), .a4(a4), .a5(a5), .a6(a6), .a7(a7), .s0(a6), .s0(a6
s0), .s1(s1), .s2(s2), .y(y));
        initial
                 begin
                         #300
                        #30; a0=1; a1=0; a2=0; a3=0; a4=0; a5=0; a6=0; a7=0; s0=0; s1=0;
s2=0;
                        #30; a0=0; a1=1; a2=0; a3=0; a4=0; a5=0; a6=0; a7=0; s0=1; s1=0;
s2=0;
                        #30; a0=0; a1=0; a2=1; a3=0; a4=0; a5=0; a6=0; a7=0; s0=0; s1=1;
s2=0;
                        #30; a0=0; a1=1; a2=0; a3=1; a4=0; a5=0; a6=0; a7=0; s0=1; s1=1;
s2=0;
                         #30; a0=0; a1=0; a2=0; a3=0; a4=1; a5=0; a6=0; a7=0; s0=0; s1=0;
s2=1;
                        #30; a0=0; a1=1; a2=0; a3=0; a4=0; a5=1; a6=0; a7=0; s0=1; s1=0;
s2=1;
                        #30; a0=0; a1=0; a2=1; a3=0; a4=0; a5=0; a6=1; a7=0; s0=0; s1=1;
s2=1;
                        #30; a0=0; a1=0; a2=0; a3=0; a4=0; a5=0; a6=0; a7=1; s0=1; s1=1;
s2=1;
                 end
```

E-) $F(A,B,C,D)=\sum (0,1,3,4,7,8,10,11,15)$ Function

Schematic

 

SystemVerilog

```
`timescale 1ns / 1ps
module SpecialFunction( input A, B, C, D, output y );
  wire notD;
  not not0( notD, D );
  MuxEightToOne mux0( 1, notD, D, 1, notD, 0, 0, 1, A, B, C, y );
endmodule
```

Testbench

```
`timescale 1ns / 1ps
module SpecialFunction tb;
  reg A, B, C, D;
  wire y;
  SpecialFunction uut( .A(A), .B(B), .C(C), .D(D), .y(y) );
  initial
    begin
      #300
      #30; A=0; B=0; C=0; D=0;
      #30; A=1; B=0; C=0; D=0;
      #30; A=0; B=1; C=0; D=0;
      #30; A=1; B=1; C=0; D=0;
      #30; A=0; B=0; C=1; D=0;
      #30; A=1; B=0; C=1; D=0;
      #30; A=0; B=1; C=1; D=0;
      #30; A=1; B=1; C=1; D=0;
      #30; A=0; B=0; C=0; D=1;
      #30; A=1; B=0; C=0; D=1;
      #30; A=0; B=1; C=0; D=1;
      #30; A=1; B=1; C=0; D=1;
      #30; A=0; B=0; C=1; D=1;
      #30; A=1; B=0; C=1; D=1;
      #30; A=0; B=1; C=1; D=1;
      #30; A=1; B=1; C=1; D=1;
    end
```